



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM IV) THEORY EXAMINATION 2024-25
NETWORKS ANALYSIS & SYNTHESIS

TIME: 3 HRS

M.MARKS: 70

Note: Attempt all Sections. In case of any missing data; choose suitably.

SECTION A

1. Attempt all questions in brief.




02 x 7 = 14

Q no.	Question	CO	Level
a.	Define Link and co-tree.	1	K2
b.	State reciprocity theorem.	2	K2
c.	Differentiate between natural response and force response.	3	K2
d.	Derive condition for maximum power transfer.	2	K2
e.	State the compensation theorem.	2	K2
f.	Discuss the properties of RC driving point function.	4	K2
g.	Differentiate between active filter and passive filter.	5	K2

SECTION B

2. Attempt any three of the following:

07 x 3 = 21

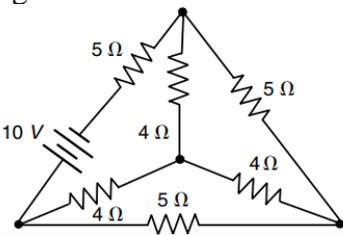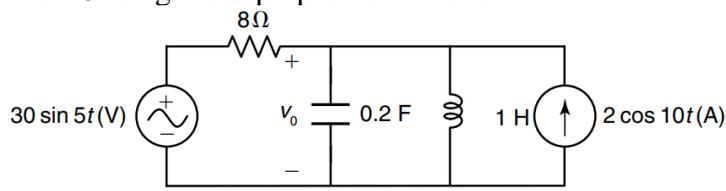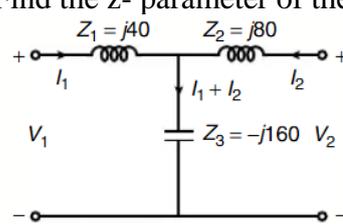Q no.	Question	CO	Level
a.	Write the incidence matrix and cut-set matrix for the network shown in figure. 	1	K2
b.	Find V_0 using the superposition theorem. 	2	K3
c.	A constant voltage of 100V is applied at $t = 0$ to a RC series circuit having $R = 5M\Omega$, $C = 20\mu F$. Assuming no initial charge to the capacitor, find current i and the voltage across R and C.	3	K3
d.	Find the z- parameter of the given network shown in figure. 	4	K3
e.	Design a constant K type low pass filter of 2000Hz and a zero-frequency characteristics impedance of 200Ω . Draw T and π section of the filter.	5	K4



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM IV) THEORY EXAMINATION 2024-25
NETWORKS ANALYSIS & SYNTHESIS

TIME: 3 HRS

M.MARKS: 70

b.	<p>The circuit shown in figure consist of resistance, inductance and capacitance in series with 100V constant source. When the switch is closed t=0, find the transient current.</p>	3	K3

6. Attempt any one part of the following:

07 x 1 = 07

Q no.	Question	CO	Level
a.	<p>Find transmission parameter of network in figure. Further prove that $AD - BC = 1$</p>	4	K3
b.	<p>Determine the Y- Parameter for the network shown in figure.</p>	4	K3

7. Attempt any one part of the following:

07 x 1 = 07

Q no.	Question	CO	Level
a.	<p>Test whether the following polynomial is Hurwitz or not.</p> $F(s) = \frac{2s^4 + 6s^3 + 11s^2 + 10s + 5}{s^4 + 5s^3 + 8s^2 + 9s + 6}$	5	K4
b.	<p>Find Cauer form -I and Cauer form -II of the following</p> $Z(s) = \frac{s(s^2 + 3)(s^2 + 5)}{(s^2 + 2)(s^2 + 4)}$	5	K4